

**Al Mansoura University**

**Faculty of Engineering**

**Electronics and Communications Dept.**

**2<sup>nd</sup> Year Students**

**Logic Circuit 2**

**First Semester 2013**

**Prepared By: Dr. Muhammad Morsy**

**Chapter 1: Latches**


**Lecture No. 1**

## 1.1-Latches.

- ✓ The latch is a type of **temporary storage** device that has **two stable** states (**bistable**) and is normally placed in a category separate from that of flip-flops.
- ✓ Latches are similar to flip-flops because they are **bistable** devices that can **reside** in either of **two states** using a **feedback arrangement**, in which the outputs are connected back to the opposite inputs.
- ✓ The main difference between **latches** and **flip-flops** is in the method used for **changing** their state.

 
### 1.2- The S-R (SET-RESET) Latch:

- ✓ A latch is a type of **bistable** logic device or **multivibrator**.
- ✓ An **active-HIGH** input S-R (SET- RESET) latch is formed with two cross-coupled **NOR** gates, as shown in Figure 1.1(a).



 
**(a) Active-HIGH input S-R latch**

- ✓ An **active-LOW** input S-R latch is formed with **two cross-coupled NAND** gates, as shown in Figure 1.1 (b).



**(b) Active-LOW input  $\bar{S}$ - $\bar{R}$  latch**


- ✓ Notice that the **output** of each gate is connected to an input of the **opposite gate**.
- ✓ This produces the **regenerative feedback** that is characteristic of all **latches** and **flip-flops**.
- ✓ To **explain** the operation of the latch, we will use the **NAND** gate S-R latch in Figure 1.1 (b).
- ✓ This latch is **redrawn** in Figure 1.2 with the **negative-OR** equivalent symbols used for the **NAND** gates.

 

**Figure (1.2)**

 
- ✓ This is done because **LOWs** on the  $\bar{S}$  and  $\bar{R}$  lines are the activating inputs.
- ✓ The latch in Figure 1-2 has **two inputs**,  $\bar{S}$  and  $\bar{R}$ , and **two outputs**,  $Q$  and  $\bar{Q}$ .
- ✓ Let's start by **assuming that** both inputs and the  $Q$  output are **HIGH** as shown in Figure (1.3).






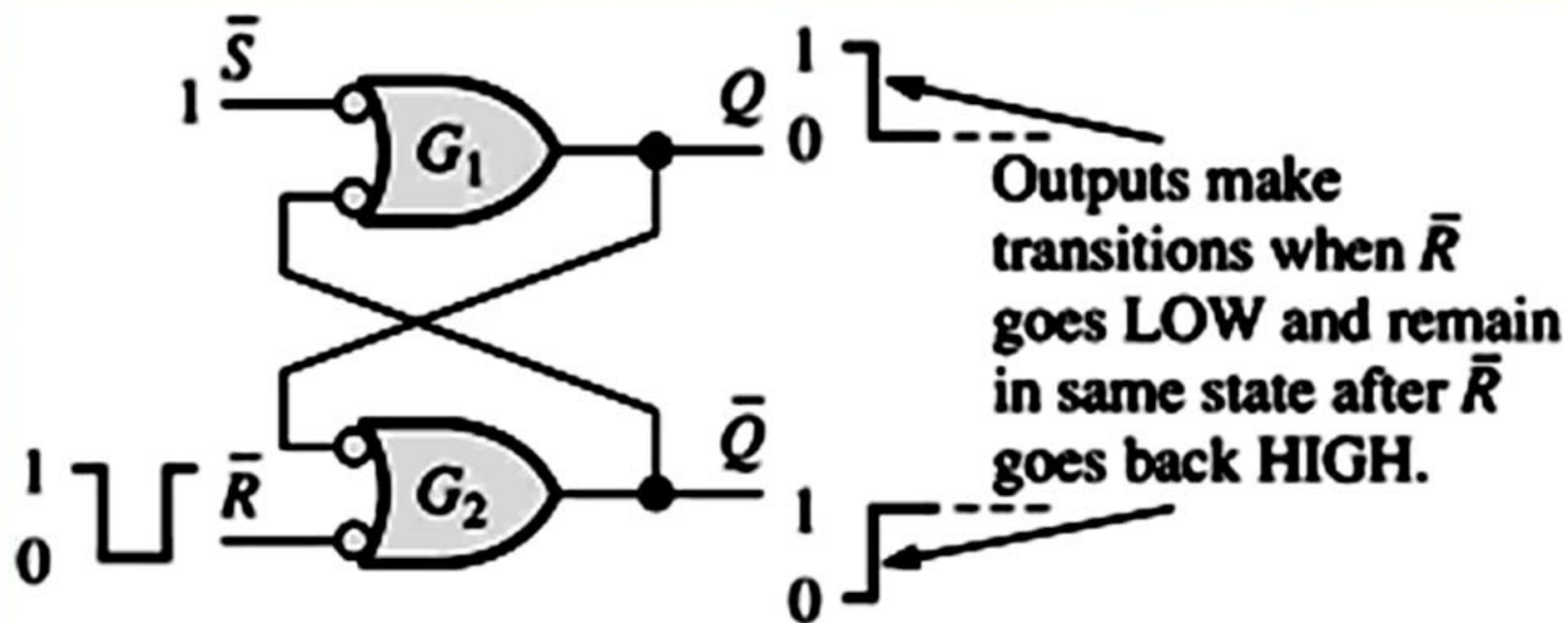**HIGHS on both inputs**

- ✓ Since the **Q output** is connected back to an input of gate  $G_2$ , and the  $\overline{R}$  input is **HIGH**, the output of  $G_2$ ,  $\overline{Q}$  must be **LOW**.
- ✓ This **LOW** output is coupled back to an input of gate  $G_1$  ensuring that its output is **HIGH**.
- ✓ When the Q output is **HIGH**, the latch is in the **SET** state.
- ✓ It will remain in this state **indefinitely** until **LOW** is temporarily applied to the  $\overline{R}$  input.
- ✓ With a **LOW** on the  $\overline{R}$  input and a **HIGH** on  $\overline{S}$ , the output of gate  $G_2$  is forced **HIGH**.



 
- ✓ This **HIGH** on the  $\overline{Q}$  output is coupled back to an input of  $G_1$ , and since the S input is **HIGH**, the output of  $G_1$  goes **LOW**.
- ✓ This **LOW** on the Q output is then coupled back to an input of  $G_2$ , ensuring that the  $\overline{Q}$  output remains **HIGH** even when the **LOW** on the  $\overline{R}$  input is **removed**.




**No transitions occur  
because latch is  
already RESET.**

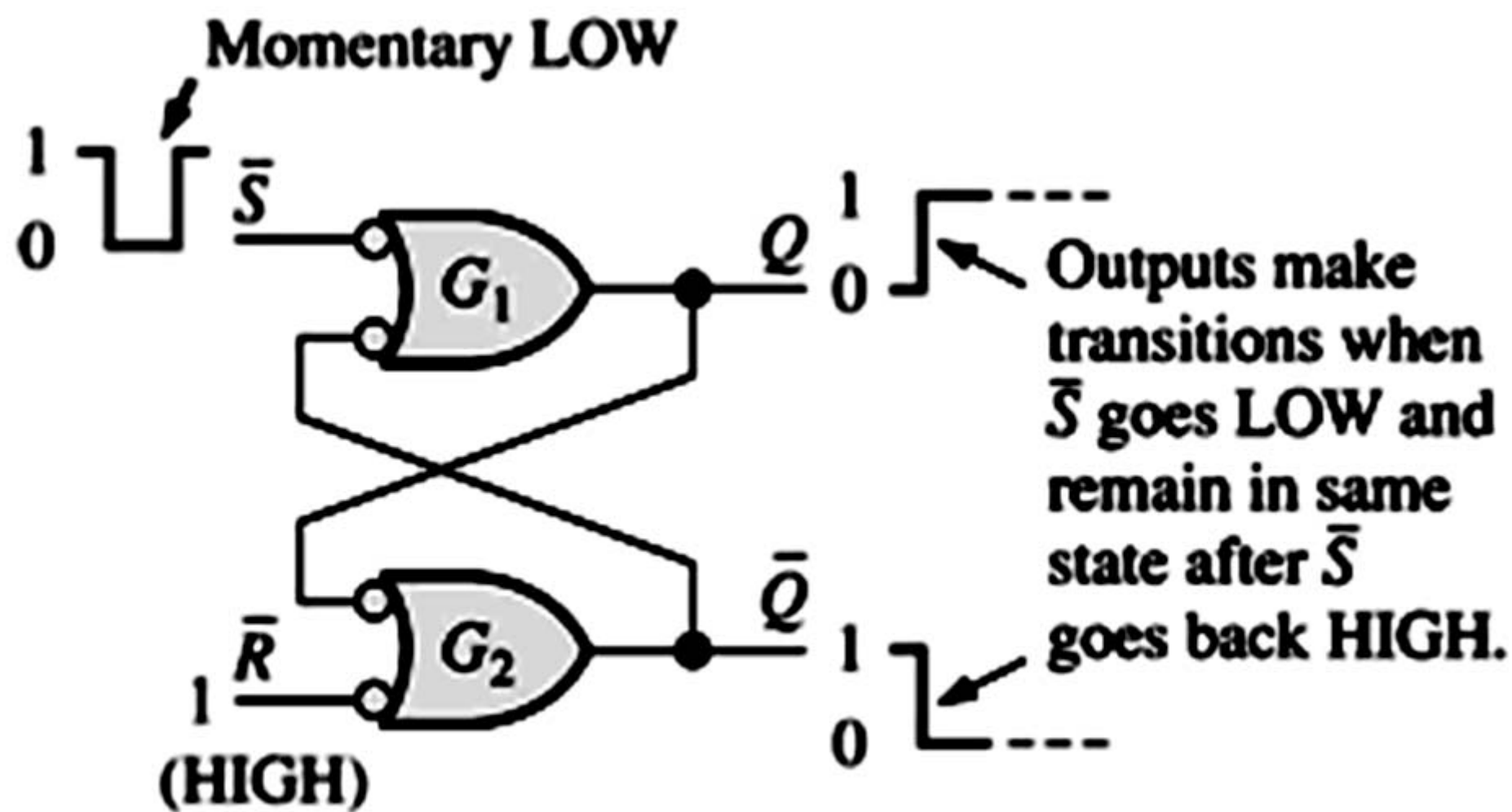**Latch starts out RESET ( $Q = 0$ ).**

- ✓ When the **Q output** is **LOW**, the latch is in the **RESET** state.
- ✓ Now the latch remains indefinitely in the **RESET** state until a **LOW** is applied to the S input.
- ✓ In **normal operation**, the **outputs** of a latch are always **complements** of each other.




**Latch starts out RESET ( $Q = 0$ ).**

 

 **Latch starts out SET ( $Q = 1$ ).**



- ✓ An **invalid condition** in the operation of an **active-LOW** input S-R latch occurs when **LOWs** are applied to **both**  $\bar{S}$  and  $\bar{R}$  at the **same time**.



**Simultaneous LOWs on both inputs**


- ✓ As long as the **LOW** levels are **simultaneously held on** the inputs, both the Q and  $\bar{Q}$  outputs are forced **HIGH**, thus **violating** the basic complementary operation of the outputs.
- ✓ Also, if the **LOWs** are released simultaneously, both outputs will attempt to go **LOW**.
- ✓ Since there is always **some small difference** in the **propagation delay time** of the gates, one of the gates will dominate in its transition to the **LOW** output state.

✓ This, in turn, **forces** the output of the **slower gate** to remain **HIGH**.


✓ In this situation, you cannot **reliably predict** the **next state** of the latch.

Table (1.1) Truth table for an active-LOW input  $\bar{S}$   $\bar{R}$  latch.

<b>Inputs</b>		<b>Outputs</b>		<b>Comments</b>
$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$	
1	1	NC	NC	<b>No Change.</b>
0	1	1	0	Latch <b>SET</b>
1	0	0	1	Latch <b>Reset</b>
0	0	1	1	<b>Invalid condition</b>

 


**(a) Active-HIGH input  
S-R latch**

 

**(b) Active-LOW input  
 $\bar{S}$ - $\bar{R}$  latch**

**Figure (1.4) Logic symbols for the S-R and  $\bar{S}$ - $\bar{R}$  latch.**

 **Example (1.1):** If the S and R waveforms in the Figure are applied to the inputs of the  $\bar{S}$ - $\bar{R}$  latch, determine the waveform that will be observed on the Q output. Assume that Q is initially **LOW**.



## State Table


Interval	$\bar{S}$	$\bar{R}$	State	Q
0	1	1	Old value, NC	0
1	0	1	Set	1
2	1	1	NC	1
3	1	0	Reset	0
4	1	1	NC	0
5	0	1	Set	1
6	1	1	NC	1

<b>6</b>	<b>1</b>	<b>1</b>	<b>NC</b>	<b>1</b>
<b>7</b>	<b>1</b>	<b>0</b>	<b>Reset</b>	<b>0</b>
<b>8</b>	<b>1</b>	<b>1</b>	<b>NC</b>	<b>0</b>
<b>9</b>	<b>1</b>	<b>0</b>	<b>Reset</b>	<b>0</b>
<b>10</b>	<b>1</b>	<b>1</b>	<b>NC</b>	<b>0</b>
<b>11</b>	<b>0</b>	<b>1</b>	<b>Set</b>	<b>1</b>
<b>12</b>	<b>1</b>	<b>1</b>	<b>NC</b>	<b>1</b>
<b>13</b>	<b>0</b>	<b>1</b>	<b>Set</b>	<b>1</b>
<b>14</b>	<b>1</b>	<b>1</b>	<b>NC</b>	<b>1</b>



 
### 1.3- The Gated S-R Latch.

- ✓ A **gated latch** requires an **enable input**, **EN** (G is also used to designate an enable input). The logic diagram and logic symbol for a gated S-R latch are shown in Figure (1.5).



**(a) Logic diagram**




 

**(b) Logic symbol**


- ✓ The S and R **inputs control** the state to which the latch will go when a **HIGH level** is applied to the **EN input**.
- ✓ The latch **will not** change until **EN** is **HIGH**; but as long as it remains **HIGH**, the output is **controlled** by the state of the S and R inputs.
- ✓ In this circuit, the **invalid state** occurs when both S and R are **simultaneously HIGH**.

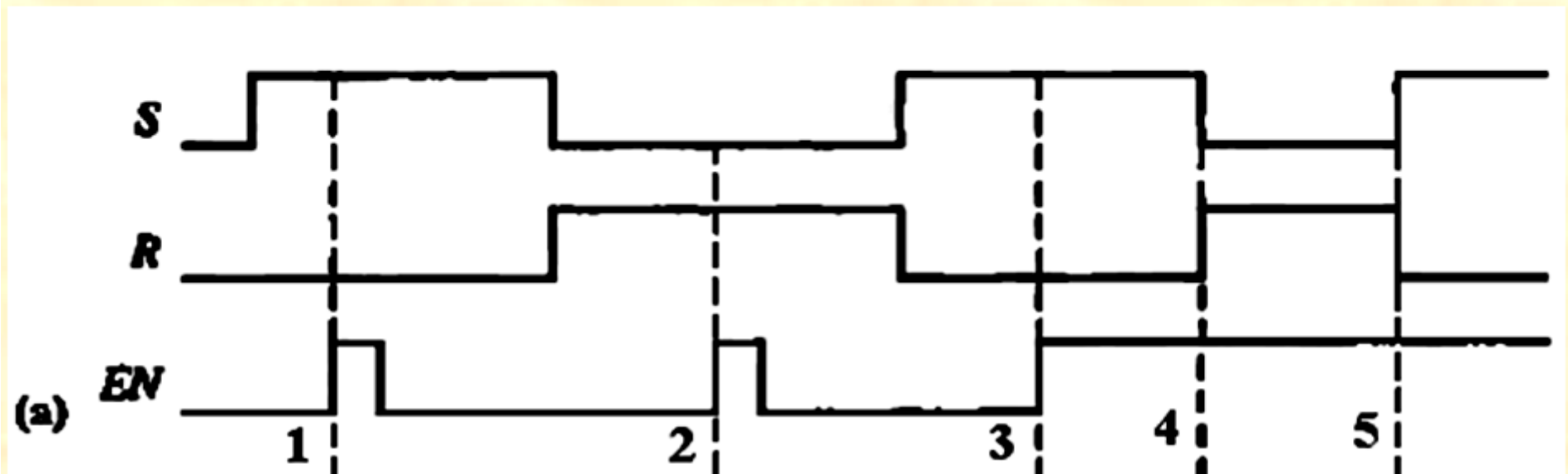**Example (1.2):** Determine the Q output waveform if the inputs shown in the Figure are applied to a gated S-R latch that is initially **RESET**.



## State Table

EN	S	R	State	Q
EN0	X	X	Old	0
EN1	1	0	Set	1
EN2	0	1	Reset	0
EN3	1	0	Set	1
EN4	0	1	Reset	0
EN5	1	0	Set	1

 


- ✓ When S is **HIGH** and R is **LOW**, a **HIGH** on the EN input **sets** the latch.
- ✓ When S is **LOW** and R is **HIGH**, a **HIGH** on the EN input **resets** the latch.

 
#### 1.4- The Gated D Latch.

- ✓ Another type of **gated latch** is called the D **latch**.
- ✓ It **differs** from the S-R latch because it has **only one input** in addition to **EN**. This input is called the **D (data)** input.

- ✓ Figure (1.6) contains a logic diagram and logic symbol of a D latch.



(a) Logic diagram

 


**(b) Logic symbol**

**Figure (1.6) A gated D latch**

- ✓ When the **D** input is **HIGH** and the **EN** input is **HIGH**, the latch will **Set**.
- ✓ When the **D** input is **LOW** and **EN** is **HIGH**, the latch will **Reset**.
- ✓ Stated another way, the **output** **Q** **follows** the input **D** when **EN** is **HIGH**.

 **Example (1.3):** Determine the **Q** output waveform if the inputs shown in the Figure are applied to a gated D latch. which is **initially RESET**.







- ✓ When  $D$  is **HIGH** and  $EN$  is **HIGH**,  $Q$  goes **HIGH**.
- ✓ When  $D$  is **LOW** and  $EN$  is **HIGH**,  $Q$  goes **LOW**.
- ✓ When  $EN$  is **LOW**, the state of the latch is **not affected** by the  $D$  input.

 
 
### 1.5-Edge Triggered Flip-Flop.

- ✓ An **edge-triggered flip-flop** changes state either at the **positive** edge (rising edge) or at the **negative** edge (falling edge) of the clock pulse and is **sensitive** to its inputs only at **this transition** of the clock.
- ✓ **Three** types of edge-triggered flip-flops are covered in this section: S-R, D, and J-K.
- ✓ Although the **S-R flip-flop** is not available in **IC** form, it is the basis for the D and J-K flip-flops.
- ✓ The **logic symbols** for all of these flip-flops are shown in Figure (1.7).



- ✓ Notice that **each type** can be either **positive** edge-triggered (**no bubble** at C input) or **negative edge** triggered (bubble at C input).
- ✓ The key to identifying an edge triggered flip-flop by its logic symbol is the **small triangle** inside the block at the **clock (C) input**.
- ✓ This triangle is called the dynamic input indicator.



(a) S-R

  

(b) D

  

(c) J-K